

Year 4

Electricity

Electrical Circuits and Conductors: Companion Project Ancient Civilizations

	Date 1:	Date 2:
1. Name three items that need electricity to work.		
2. Name some of the components that could make a simple series circuit.		
3. What happens if there is a break in a circuit?		
4. What does a switch do in a circuit?		
5. What does conduct mean?		
6. Name a material that conducts electricity.		
7. What does insulate mean?		
My questions about electricity:		
This is what I want to find out/do:		